

Experiment 0 : Combinational Circuits - 1

Mayur Ware, 19D070070

EE-214, WEL, IIT Bombay

January 28, 2021

Overview of the experiment


- The purpose of the experiment is to make a digital device which implements the given combinational Circuit.
Combinational Circuit : The circuit has 8 inputs $x_7, x_6, x_5, x_4, \dots, x_0$ and two outputs y_1, y_0 . The output bit y_1 is 1 if and only if the number of input bits that are 1 is greater than the number of input bits that are 0. The output bit y_0 is the complement of y_1 .
- I used Full Adder for the calculation of sum and carry in the input for $[x_7, x_6, x_5]$ and $[x_4, x_3, x_2]$ set of bits and Half Adder for $[x_1, x_0]$. Then I used Four Bit Adder to find the exact No. of 1s in the input.
- The report contains a handmade diagram which describes my approach, some important extracts of VHDL code and the output waveforms.

Approach to the experiment

I used 2 Full Adders and 1 Half Adder in the design which give the sum and carry of the given sets of input bits. This gives output in the form of carry bits C_2, C_1 and C_0 and sum bits S_2, S_1 and S_0 . Then I Added these outputs in the form of $00C_2S_2 + 00C_1S_1 + 00C_0S_0$ with the help of Four Bit Adder which gives output $R'_3 R'_2 R'_1 R'_0$ which is the exact No. of 1s in the input bits.

Now, when the No. of 1s will exceed 4, it will be greater than the No. of 0s, then Y_1 will be 1. This implies, for 0101 0110 0111 1000, Y_1 will be 1. By using a K-MAP and setting values exceeding 1000 as Don't Cares. We get the following expression for Y_1 .

$$Y_1 = R'_3 + (R'_2 \& (R'_1 + R'_0))$$

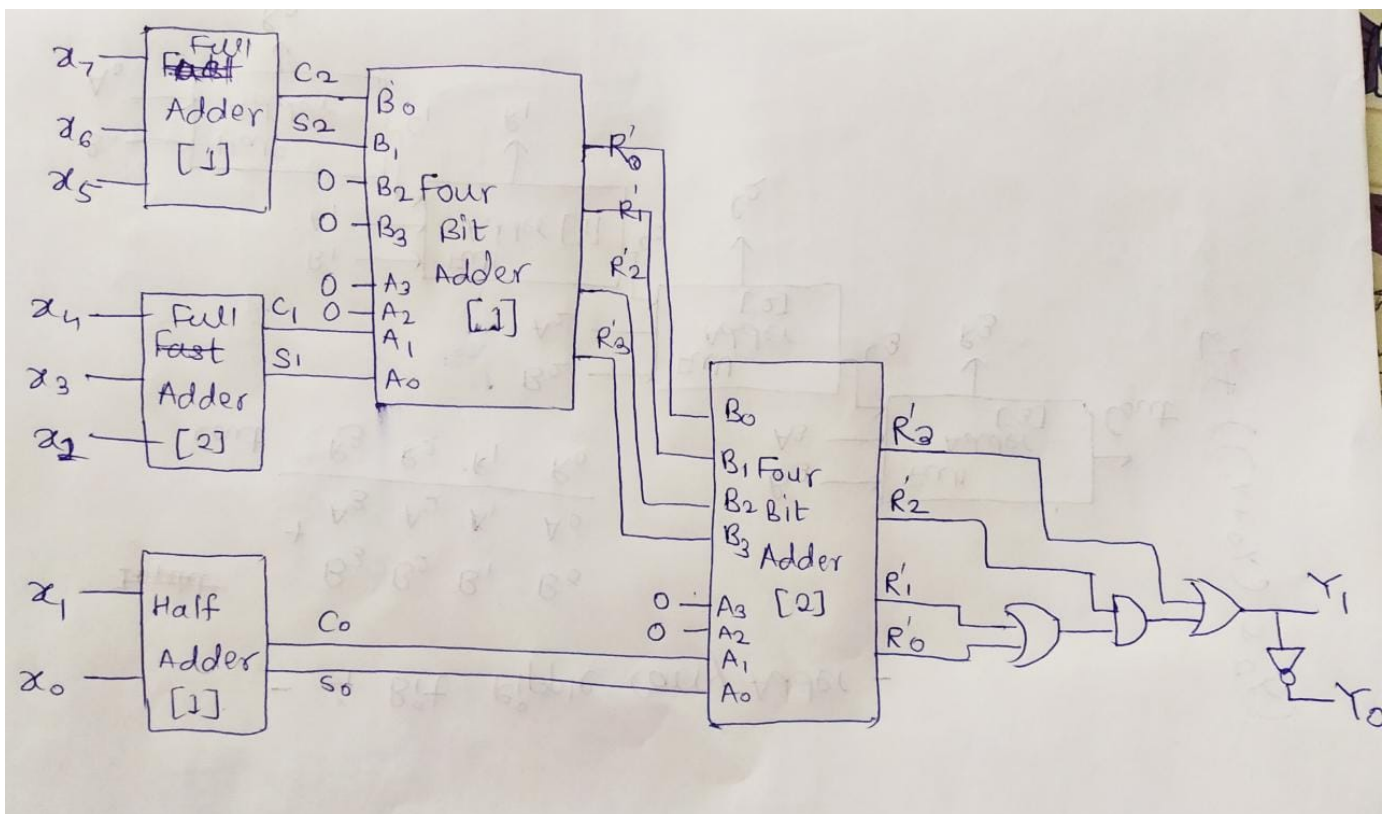

Design document and VHDL code if relevant


Full Adder :

```

entity Exp_0_EE214 is
port (X : in std_logic_vector(7 downto 0);
      Y : out std_logic_vector(1 downto 0));
end entity Exp_0_EE214;
architecture Struct of Exp_0_EE214 is
signal C2, C1, C0, S2, S1, S0, M: std_logic;
signal F4, F3, F2 : std_logic_vector(3 downto 0);
signal F1, F0 : std_logic_vector(4 downto 0);
begin
HA1: Half_Adder port map (A => X(1), B => X(0), S => S0, C => C0);
FA1: Full_Adder port map (A => X(2), B => X(3), Cin => X(4), S => S1, Cout => C1);
FA2: Full_Adder port map (A => X(5), B => X(6), Cin => X(7), S => S2, Cout => C2);
F4(3) <= '0';
F4(2) <= '0';
F4(1) <= C2;
F4(0) <= S2;
F3(3) <= '0';
F3(2) <= '0';
F3(1) <= C1;
F3(0) <= S1;
F2(3) <= '0';
F2(2) <= '0';
F2(1) <= C0;
F2(0) <= S0;          -- Assigning Appropriate bits to the Four_Bit_Adders
FBA1: Four_Bit_Adder
port map (B3 => F4(3), A3 => F3(3), B2 => F4(2), A2 => F3(2), B1 => F4(1), A1 => F3(1), B0 => F4(0), A0 =>
F3(0), R3 => F1(3), R2 => F1(2), R1 => F1(1), R0 => F1(0), Cout => F1(4));
FBA2: Four_Bit_Adder
port map (B3 => F1(3), A3 => F2(3), B2 => F1(2), A2 => F2(2), B1 => F1(1), A1 => F2(1), B0 => F1(0), A0 =>
F2(0), R3 => F0(3), R2 => F0(2), R1 => F0(1), R0 => F0(0), Cout => F0(4));
M <= F0(3) or (F0(2) and (F0(0) or F0(1)));      --Creating Signal M
Y(1) <= M;                                       -- Y1 = M
INV1: Invert_1 port map ( A => M, Y => Y(0));    -- Y0 = Y1
end Struct;

```


RTL View

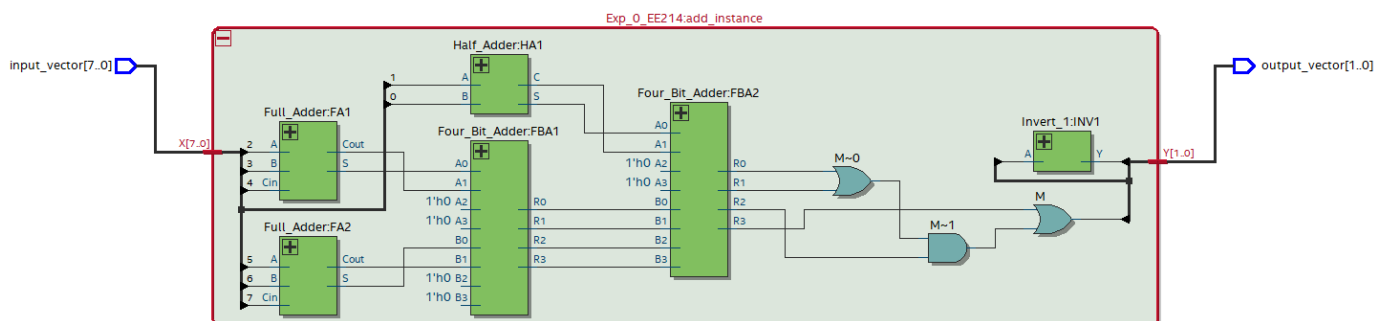


DUT Input/Output Format

X : in std_logic_vector(7 downto 0);	–Input Bit Vector
Y : out std_logic_vector(1 downto 0));	–Output Bit Vector
11101111 10 11	–Input Bit Vector, Output Bit Vector, Mask Bits

RTL Simulation

 

Gate-level Simulation

 

Krypton board*

Map the logic circuit to the Krypton board and attach the images of the pin assignment and output observed on the board (switches/LEDs).

Observations*

You must summarize your observations, either in words, using figures and/or tables.

References

None

* To be submitted after the tutorial on "Using Krypton."