

Experiment 1

Combinational Circuits - 1

Part 2

Mayur Ware, 19D070070

EE-214, WEL, IIT Bombay

February 15, 2021

Overview of the experiment

- The purpose of the experiment is to design a block which adds two 2-digit BCD numbers D1 and D2. The output will be valid a 2-digit BCD number and carry.
- I used Four_Bit_Adder multiple times for Decimal Adjusting which uses simplified K-Map equation to add 6 in non BCD cases.
- The report contains a handmade diagram which describes my approach, some important extracts of VHDL code and the output waveforms.

Approach to the experiment

For BCD Adjust, I used K-Map simplification to add 6 to the number if the number is non BCD.

Equations :

For a 4 bit number A3 A2 A1 A0,


$$P = \overline{A3} + \overline{A2} \cdot \overline{A1}$$

$$\text{Auxillary Carry(AC)} = \text{Cout} + S3 \cdot S2 + S3 \cdot S1$$

Then, For Decimal Adjust,

Using a Four_Bit_Adder add 0 AC AC 0 and S3 S2 S1 S0 which will give the appropriate output.

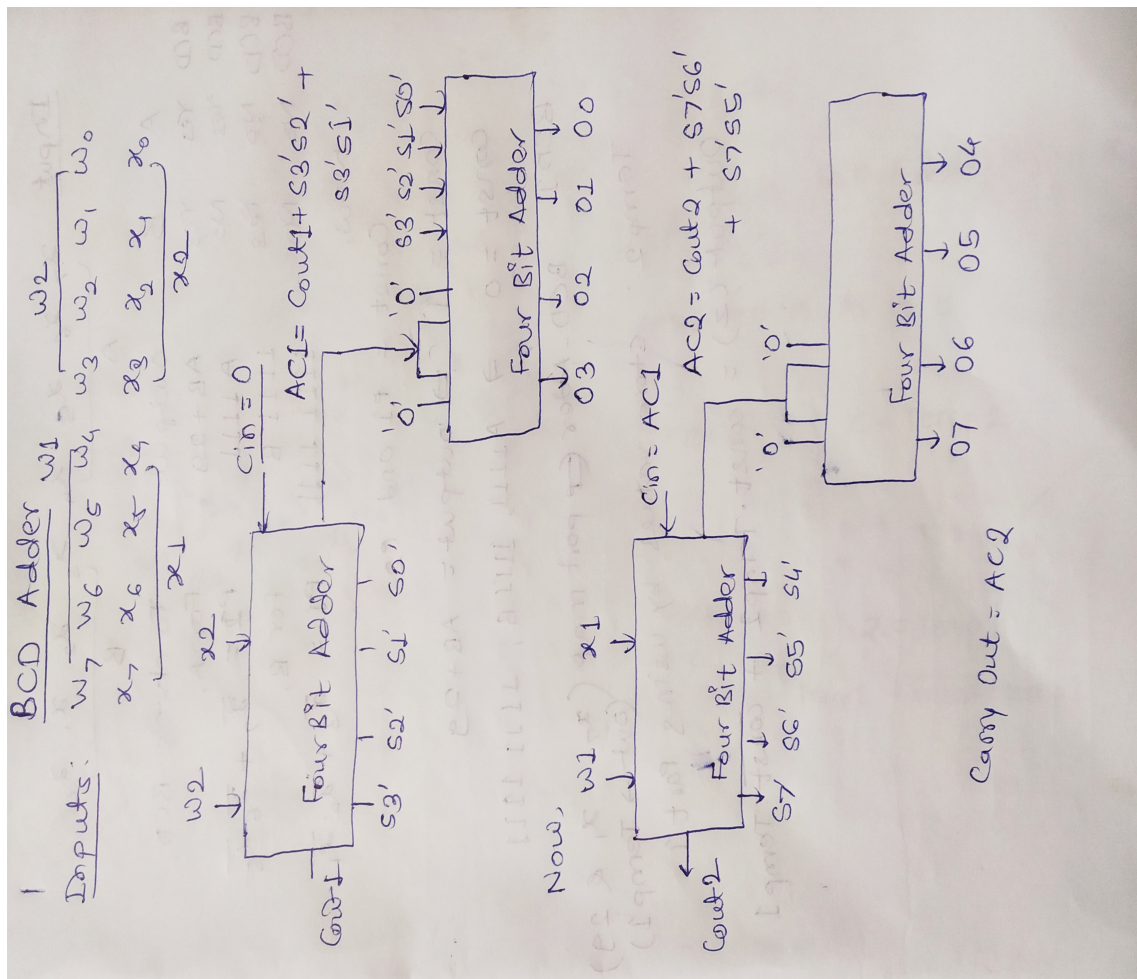The same process will repeat for most significant bytes with Auxillary Carry of previous equation as it's Carry In.



Design document and VHDL code if relevant

Main Entity :

entity Part3 is

port (W : in std_logic_vector(7 downto 0);

X : in std_logic_vector(7 downto 0);

Y : out std_logic_vector(7 downto 0);

Z : out std_logic);

end entity Part3;

OR3_1 : Or_3 port map (A= $\bar{A}C1$, B= $\bar{A}1$, C= $\bar{A}2$, Y= $\bar{A}0$);

–Eqn for calculating Auxillary Carry

Four_Bit_Adder :

component Four_Bit_Adder is


port (inp: in std_logic_vector(7 downto 0);

Cin1 : in std_logic;

outp: out std_logic_vector(4 downto 0));

end component Four_Bit_Adder;

RTL View

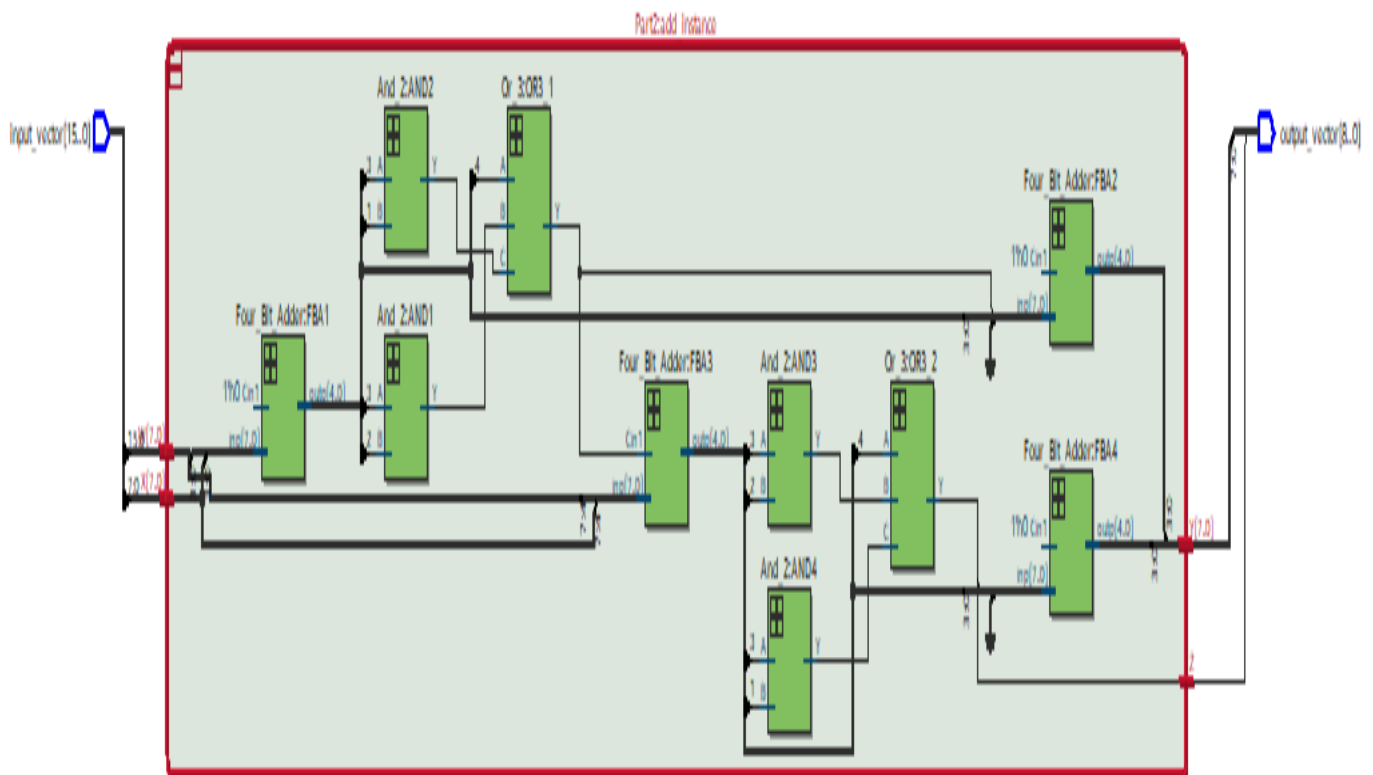

DUT Input/Output Format

W : in std_logic_vector(7 downto 0);

–Input1

X : in std_logic_vector(7 downto 0);

–Input2

Y : out std_logic_vector(7 downto 0);

–Output


Z : out std_logic);

–Carry Out


0000000000010110 000010110 11111111

–Input Bits, Output Bits, Mask Bits

RTL Simulation

 

Gate-level Simulation

 

Krypton board


Not Applicable

Observations

Not Applicable

Tiva C

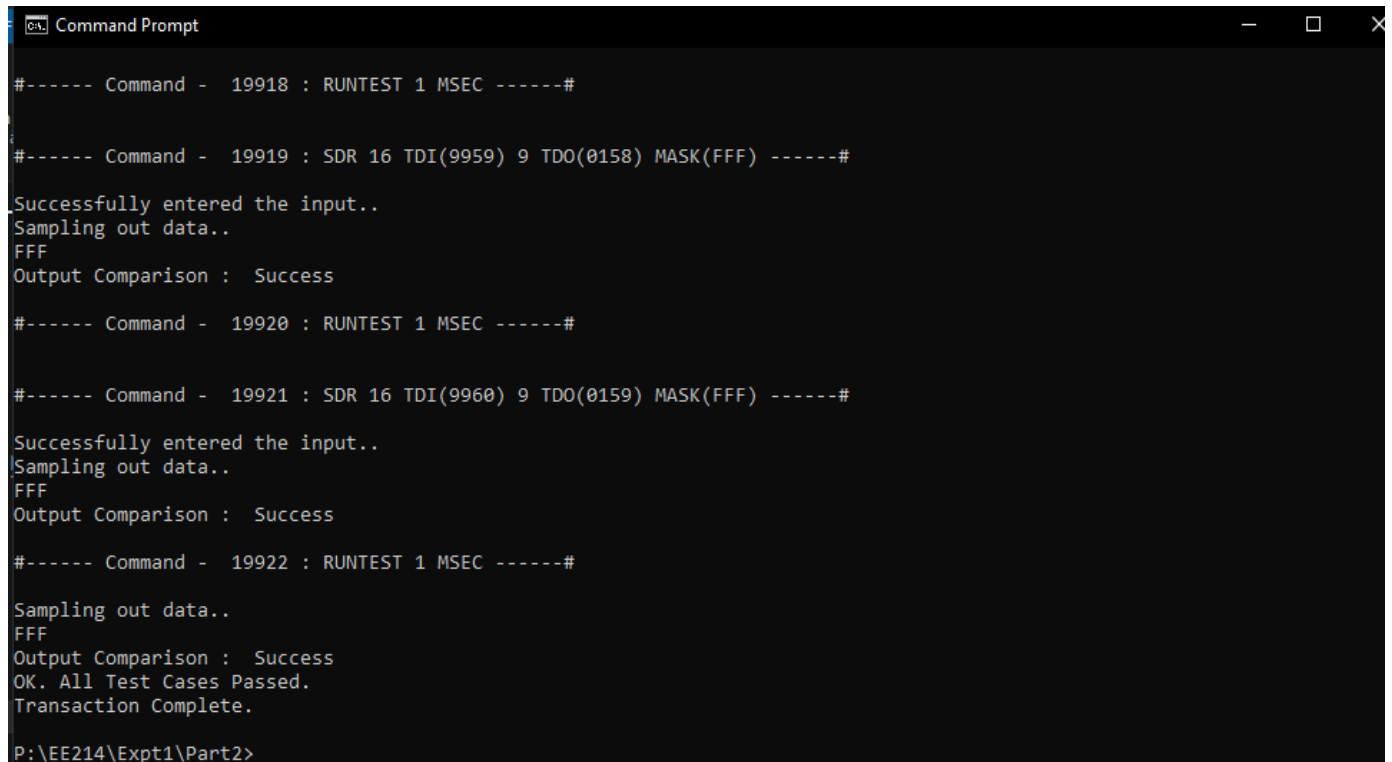After generating all 9961 testcases in in.txt, Tiva-C compiled outputs in output.txt. Image attached below shows the successful compilation.



```
#----- Command - 19918 : RUNTEST 1 MSEC -----#

#----- Command - 19919 : SDR 16 TDI(9959) 9 TDO(0158) MASK(FFF) -----#

Successfully entered the input..
Sampling out data..
FFF
Output Comparison : Success

#----- Command - 19920 : RUNTEST 1 MSEC -----#

#----- Command - 19921 : SDR 16 TDI(9960) 9 TDO(0159) MASK(FFF) -----#

Successfully entered the input..
Sampling out data..
FFF
Output Comparison : Success

#----- Command - 19922 : RUNTEST 1 MSEC -----#

Sampling out data..
FFF
Output Comparison : Success
OK. All Test Cases Passed.
Transaction Complete.

P:\EE214\Expt1\Part2>
```

References

EE 309 : Microprocessors by Prof. Dinesh Sharma Video Lectures for understanding the logic and design of BCD.